

Problems for Module 3, MC Machines:

Textbook Chap. 4: Examples: 4.6 and 4.9 (ignore the parts related to the armature reaction)

Textbook Chap. 4: Problems: 4.30, 4.31, 4.32, 4.38, and 4.39.

EXAMPLE 4.6

The dc machine (12 kW, 100 V, 1000 rpm) of Example 4.2 is connected to a 100 V dc supply and is operated as a dc shunt motor. At no-load condition, the motor runs at 1000 rpm, and the armature takes 6 amperes.

- (a) Find the value of the resistance of the shunt field control rheostat (R_{fc}).
- (b) Find the rotational losses at 1000 rpm.
- (c) Find the speed, electromagnetic torque, and efficiency of the motor when rated current flows in the armature.
 - (i) Consider that the air gap flux remains the same as that at no load.
 - (ii) Consider that the air gap flux is reduced by 5% when rated current flows in the armature because of armature reaction.
- (d) Find the starting torque if the starting armature current is limited to 150% of its rated value.
 - (i) Neglect armature reaction.
 - (ii) Consider armature reaction, $I_{f(AR)} = 0.16$ A.

EXAMPLE 4.9

A 220 V, 7 hp series motor is mechanically coupled to a fan and draws 25 amps and runs at 300 rpm when connected to a 220 V supply with no external resistance connected to the armature circuit (i.e., $R_{ae} = 0$). The torque required by the fan is proportional to the square of the speed. $R_a = 0.6 \Omega$ and $R_{sr} = 0.4 \Omega$. Neglect armature reaction and rotational loss.

- (a) Determine the power delivered to the fan and the torque developed by the machine.
- (b) The speed is to be reduced to 200 rpm by inserting a resistance (R_{ae}) in the armature circuit. Determine the value of this resistance and the power delivered to the fan.

❖ (ignore the parts related to the armature reaction)

- 4.30** A permanent magnet dc motor drives a mechanical load requiring a constant torque of $25 \text{ N} \cdot \text{m}$. The motor produces $10 \text{ N} \cdot \text{m}$ with an armature current of 10 A . The resistance of the armature circuit is 0.2Ω . A 200 V dc supply is applied to the armature terminals. Determine the speed of the motor.
- 4.31** A dc shunt motor drives an elevator load that requires a constant torque of $300 \text{ N} \cdot \text{m}$. The motor is connected to a 600 V dc supply and the motor rotates at 1500 rpm . The armature resistance is 0.5Ω .
- (a) Determine the armature current.
 - (b) If the shunt field flux is reduced by 10% , determine the armature current and the speed of the motor.
- 4.32** A dc shunt motor (50 hp , 250 V) is connected to a 230 V supply and delivers power to a load drawing an armature current of 200 amperes and running at a speed of 1200 rpm . $R_a = 0.2 \Omega$.
- (a) Determine the value of the generated voltage at this load condition.
 - (b) Determine the value of the load torque. The rotational losses are 500 watts .
 - (c) Determine the efficiency of the motor if the field circuit resistance is 115Ω .
- 4.38** A dc motor is mechanically connected to a constant-torque load. When the armature is connected to a 120 V dc supply, it draws an armature current of value 8 A and runs at 1800 rpm . The armature resistance is $R_a = 0.08 \Omega$. Accidentally, the field circuit breaks and the flux drops to the residual flux, which is only 5% of the original flux.
- (a) Determine the value of the armature current immediately after the field circuit breaks (i.e., before the speed has had time to change from 1800 rpm).
 - (b) Determine the theoretical final speed of the motor after the field circuit breaks.
- 4.39** A 600 V dc series motor has armature and field winding resistance of 0.5Ω . When connected to a 600 V supply, it operates at 500 rpm and takes 75 A . If the load torque is reduced to half, determine
- (a) The armature current.
 - (b) The speed at which it will operate.
- Assume that the flux is proportional to current and neglect armature reaction.